

Quiz This Wednesday? 16

If not, Quiz next. Monday 21
014

Topic:

Ampere's Law 8
Faraday's Law 3

Example:


Find $B(r)$

all 3 regions

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{in}$$

(I) $r < R_1$ inside
(II) $R_1 < r < R_2$ middle

(III) $R_2 < r$ outside

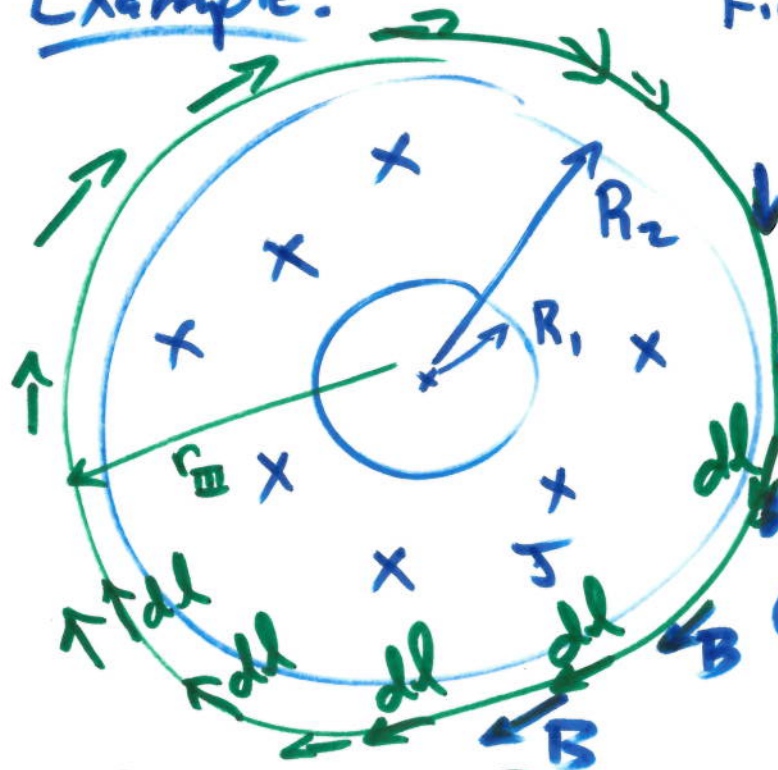

$$(III) \oint \vec{B} \cdot d\vec{l} = \mu_0 I_{in}$$

$$\oint B dl =$$

$$\vec{A} \cdot \vec{B} = AB \cos \theta$$

if $\theta = 0$

$$\vec{A} \cdot \vec{B} = AB$$

$$\oint B \, dl = \mu_0 I_{in}$$

$$B \, 2\pi r = \mu_0 (J A_{in})$$

$$J = \frac{I}{\text{area}} \Rightarrow I_{in} = J A_{in}$$

$$A_{in} = \pi R_2^2 - \pi R_1^2 = \text{the area with } J \text{ in it.}$$

$$B = \frac{\mu_0 J (\pi R_2^2 - \pi R_1^2)}{2\pi r}$$

(III)
 $r > R_2$ outside

what changes in (II)?


$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{in}$$

$$B \, 2\pi r = \mu_0 J A_{in}$$

$$A_{in} = \pi r^2 - \pi R_1^2$$

$$B = \frac{\mu_0 J (\pi r^2 - \pi R_1^2)}{2\pi r}$$

Region (II)
the middle

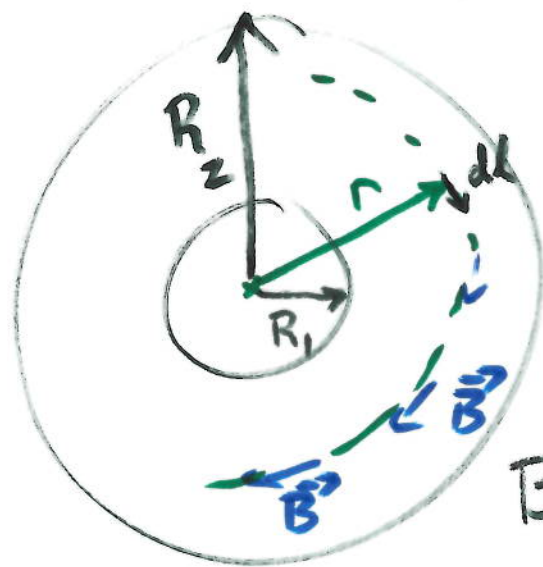


lastly, region (I)

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{in}$$

$r < R_1$

No I inside.

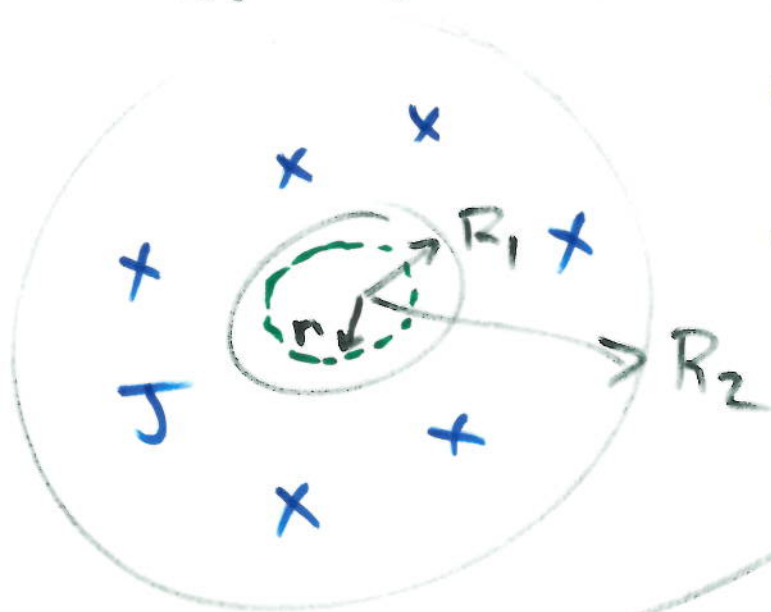

Last time: AC Circuits:

Inductor  L only $V = X_L I$

$$X_L = \omega \cdot L$$

and for a capacitor only

$$V = X_C I$$

$$X_C = \frac{1}{\omega C}$$

$$\omega = 2\pi f$$

\uparrow angular frequency


\nwarrow frequency (Hz)

X is called "reactance" unit: ohm
acts like resistance

R only is really boring.

$$V = RI \quad \text{so } X_R = R$$

In series you can combine all 3:

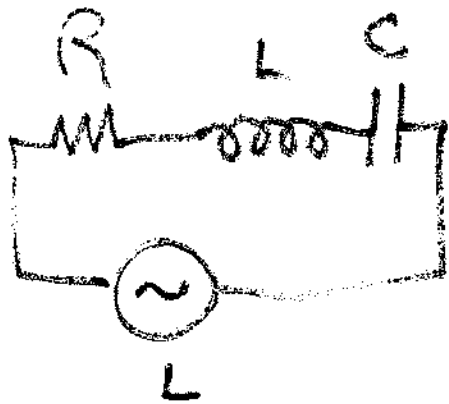


Combine together to make "Impedance"

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

so Z is minimum

when $X_L = X_C$

we call this resonance.

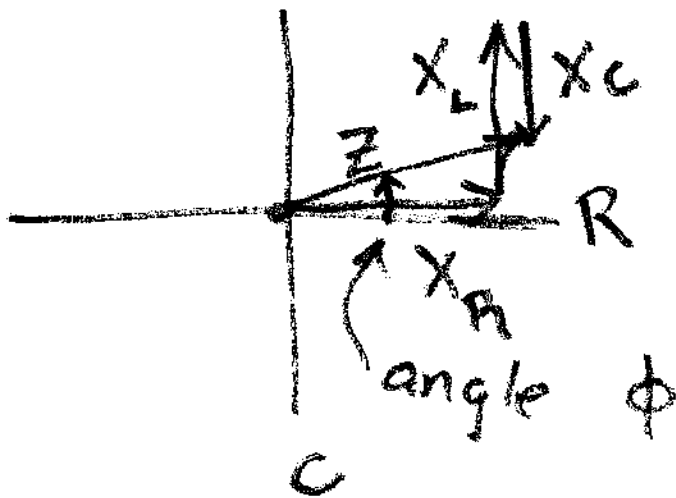

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

↑
phase shift

$$\underline{V = Z I}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

when

$$\omega = \omega^*, \quad X_L = X_C \quad \text{thus: } \omega^* L = \frac{1}{\omega^* C}$$

$$\omega^{*2} = \frac{1}{LC}$$

$$\omega^* = \frac{1}{\sqrt{LC}}$$

↑
the resonant frequency.
(angular)

$$2\pi f^* = \omega^*$$

↑
resonant
frequency

$$f^* = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

If $R = 10.0 \Omega$, and inductor $L = 1.0 \times 10^{-6} \text{ H}$
 what C do you need to $f^* = 90.7 \times 10^6 \text{ Hz}$

Then: What is Z at $90.7 \times 10^6 \text{ Hz}$?

What is Z at $90.5 \times 10^6 \text{ Hz}$

$$f^* = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} \rightarrow C = \frac{1}{(2\pi f^*)^2 L}$$

$$C = \frac{1}{(2\pi \cdot 90.7 \times 10^6)^2 \cdot 1.0 \times 10^{-6}} = 3.08 \times 10^{-12} \text{ F}$$

at resonance, $Z = R$. Duh.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


at resonance, $X_L = X_C$.

$$Z = 10 \Omega \text{ at } 90.7 \text{ MHz.}$$

$$\text{at } 90.5 \text{ MHz, } X_L = \omega L = 568 \Omega$$

$$X_C = \frac{1}{\omega C} = 572 \Omega$$
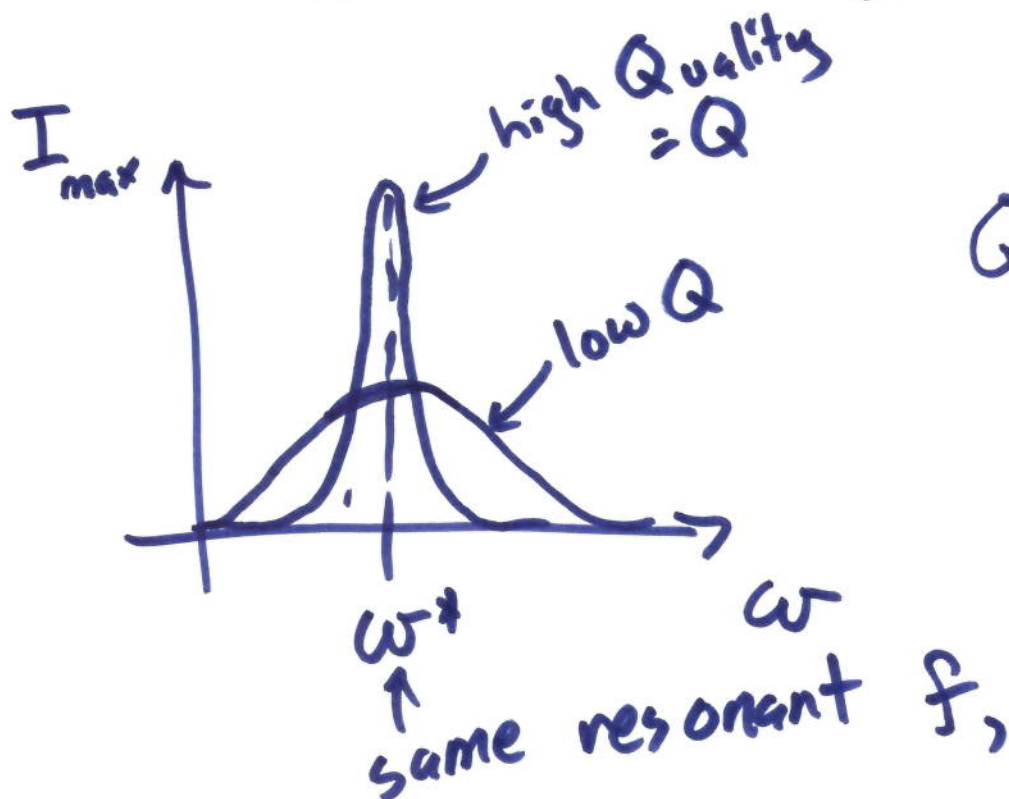
$$Z = 10.6 \Omega \text{ (very slight difference)}$$



$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{\omega^*}{\Delta \omega}$$

width of peak