

Physics 201

Day 16

No lab Friday.

Note: March 30 is a holiday
we will review for exam 2 in lecture.

Exam 2 will occur at end of week 10
April 6th.

Some Items for Exam 2:

★ - Ampere's Law

★ - Faraday's Law

Lenz's law for 1 point only
right hand rules

Sketch \vec{B}

3 Magnetic materials

LR circuits ...


RC Circuits - -

I will
show
you ↓ LC Circuit

AC Circuits

maybe electromagnetic waves (light)

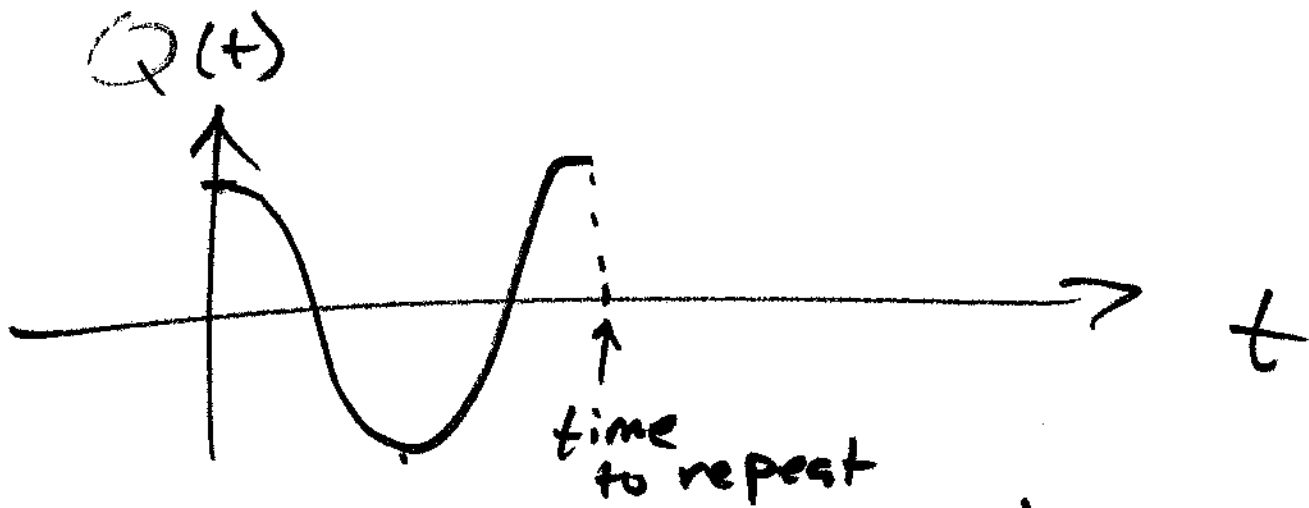$2\pi f = \omega$ — the angular frequency
 ↑
 the frequency



$t = T = \text{the period}$


$$f = \frac{1}{T}$$

$$T = \frac{2\pi}{\omega} \quad 2\pi f = \omega$$

AC Circuits


the voltage is a function of time
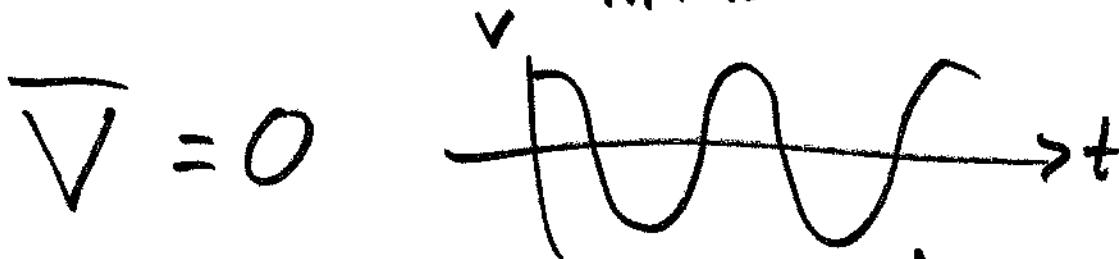
$$V = V_{\max} \cos(\underbrace{\omega t}_{\text{in radians}})$$



$$\overline{V} = 0$$

V_{rms} should be measured.

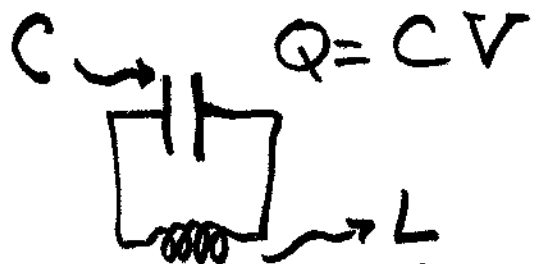

$$I = -\frac{dQ}{dt}$$

LC Circuit (No power supply needed).

$$\sum V_{\text{loop}} = 0$$

$$V_C + V_L = 0$$

$$\frac{Q(t)}{C} + L \frac{dI(t)}{dt} = 0$$

$$\rightarrow \frac{Q(t)}{C} = -L \frac{d^2 Q}{dt^2}$$

$$Q(t) = Q_{\text{max}} \cdot \cos(\omega t)$$

if $Q(t=0) = Q_{\text{max}}$
so all Q on C at
the beginning.

$$\frac{d^2 Q}{dt^2} = -Q_{\text{max}} \cos(\omega t) \omega^2$$

$$\cancel{Q_{\text{max}}} \frac{\cancel{\cos(\omega t)}}{C} = -L (-\cancel{Q_{\text{max}}}) \cancel{\cos(\omega t)} \omega^2$$


$$\frac{1}{LC} = \omega^2$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\sqrt{V^2(t)} = V_{rms}$$

$$\sqrt{V_{max}^2 \cos^2(\omega t)} = V_{rms}$$
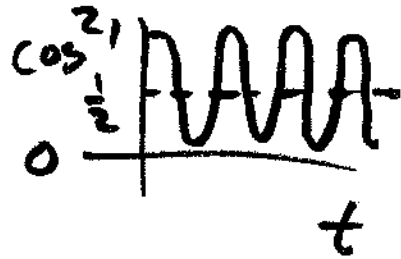
$$V_{max} \sqrt{\cos^2(\omega t)} = V_{rms}$$



$$\frac{V_{max}}{\sqrt{2}} = V_{rms} \leftarrow \text{this is our 120V ac in the USA.}$$

Same with current.

$$I(t) = I_{max} \cos(\omega t)$$

$$\text{measure } I_{rms} = \frac{I_{max}}{\sqrt{2}}$$


The resistor

$$V = RI$$

$$V_{max} \cos(\omega t) = R I_{max} \cos(\omega t)$$

$$\frac{V_{max}}{R} = I_{max} \quad \text{and} \quad \frac{V_{rms}}{R} = I_{rms}$$

the Capacitor:

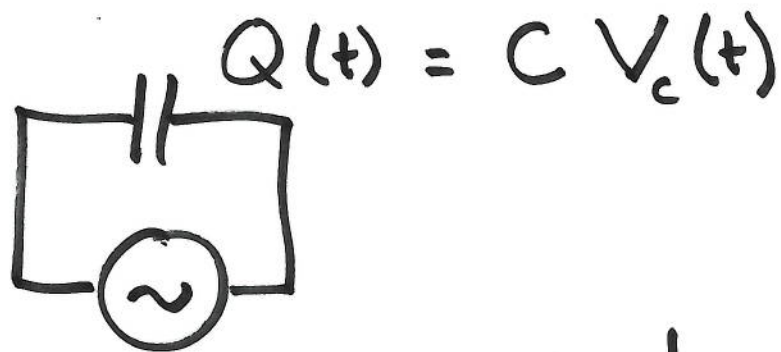


↑ AC power supply,
or function generator
has V_{\max} and ω .

$$I(t) = \frac{dQ(t)}{dt} \quad \text{if } I(t) = I_{\max} \cos(\omega t)$$

$$\text{then } Q(t) = \int_0^t I(t) dt = \int I_{\max} \cos(\omega t) dt$$

$$Q(t) = I_{\max} \frac{\sin(\omega t)}{\omega}$$
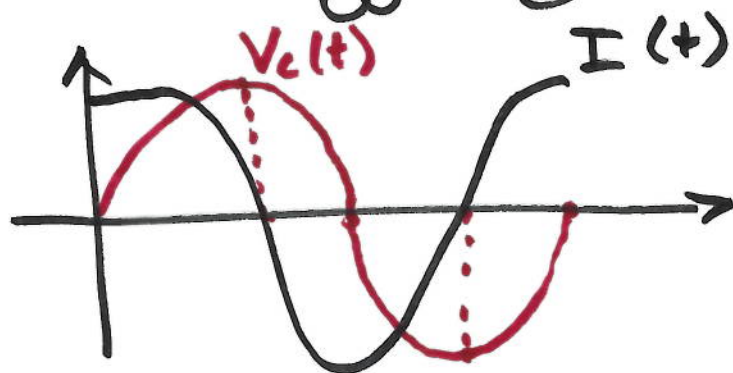
$$V_c(t) = \frac{I_{\max}}{\omega} \cdot \frac{1}{C} \sin(\omega t)$$



I leads the V
in a Capacitive
Circuit by $\frac{\pi}{4}$ radians

$$V_{\max} = X_C I_{\max}$$


↑
the reactance of Capacitor

(Note: has unit of Ω acts like a frequency dependent resistor).


$$V_{\max} = I_{\max} \left(\frac{1}{\omega C} \right)$$

$$\boxed{\frac{1}{\omega C} = X_C}$$

high ω has low X .

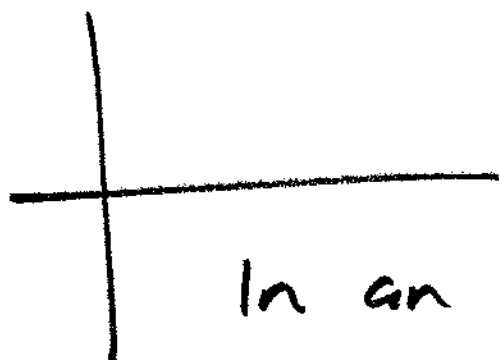

In an Inductor only

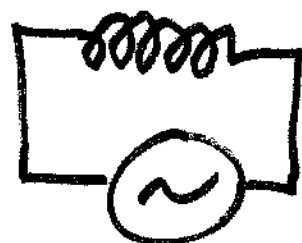

$$X_L = \omega \cdot L$$

at large ω , high resistance

I lag behind V in inductive circuit also by $\frac{\pi}{2}$ radians.

$$V_L = -L \frac{dI(t)}{dt}$$

assume
 $I(t) = I_{\max} \cos(\omega t)$