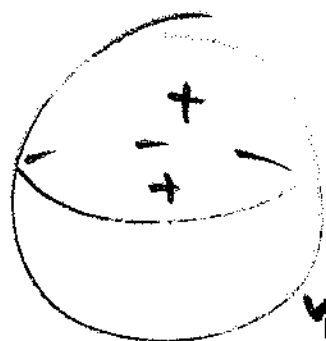


Super position:



Can
= hole




P

ρ
 V_2

$$+Q_1 = \rho V_1$$

$$-Q_2 = \rho V_2$$

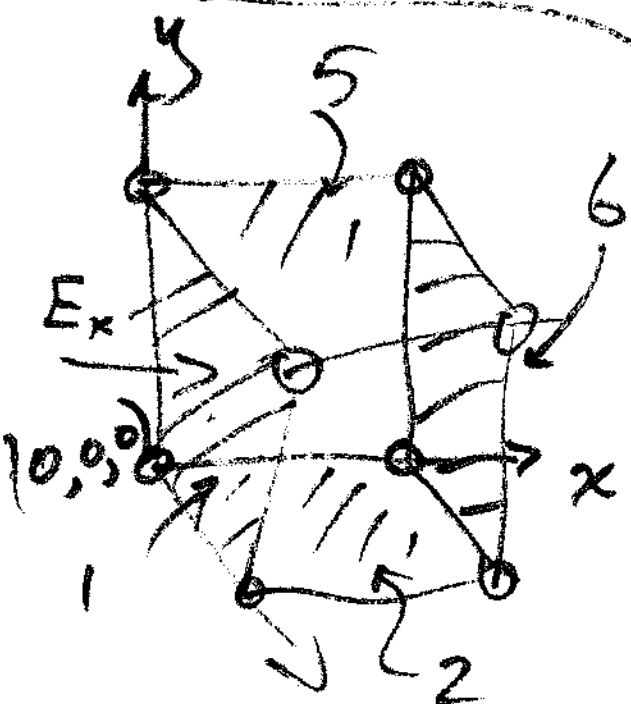

$$\vec{E} = (a + bx)\hat{i} + c\hat{j}$$

$$\Phi_E = \underbrace{\Phi_{E_1} + \Phi_{E_6}}_{\text{yes}} + \underbrace{\Phi_{E_2} + \Phi_{E_5}}_{=0}$$

$$\Phi_{E_1} = E_1 A \cos \theta = a L^2 \cos(180^\circ) = -a L^2$$

$$\Phi_{E_6} = E_6 A \cos \theta = (a + bL) L^2 \cos(0) =$$

$$\text{answer} = b L^3$$

Quiz 1.0


Topic: { Point Q: \vec{E} or \vec{F} 19
Gauss' Law 17

Day: Mon Next
Wed Next

No Q Next Week

I want a Gauss' law Quiz, too ✓

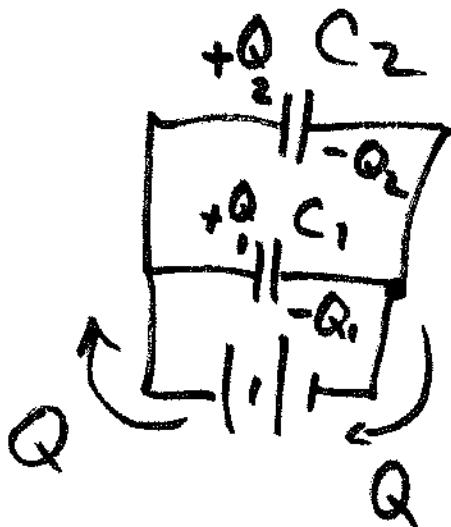Equivalent Capacitors: Series and Parallel



$$V = V_1 = V_2$$

$$Q = CV$$

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$Q = C_{\text{equiv}} V$$

equivalent



$$Q = Q_1 + Q_2$$

Find C_{equiv} given: C_1 and C_2 .

$$C_{\text{equiv}} \cancel{V} = C_1 \cancel{V} + C_2 \cancel{V}$$

$$C_{\text{equiv}} = C_1 + C_2$$

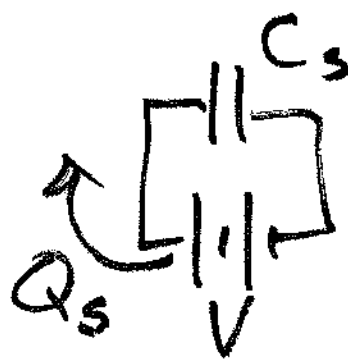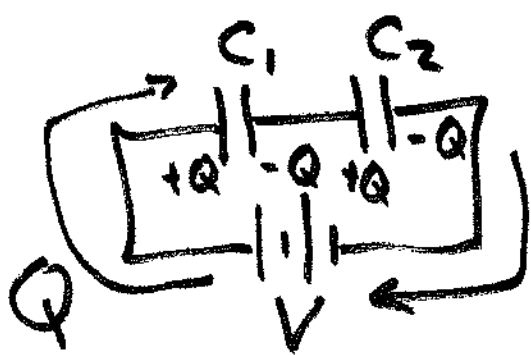for R: $R_{\text{equiv}} = \frac{R_1 R_2}{R_1 + R_2}$
They differ!



$$Q = Q_s$$

$$Q_s = C_s V$$

$$V_1 + V_2 = V$$

$$Q = C_s V$$

$$Q = C_1 V_1$$

$$Q = C_2 V_2$$

$$\frac{Q}{C_s} = V$$

$$Q = C_1 V_1$$

$$Q = C_2 V_2$$

$$\frac{Q}{C_1} + \frac{Q}{C_2} = \frac{Q}{C_s}$$

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_s}$$

$$\frac{1}{C_1} + \frac{1}{C_2} + \dots = \frac{1}{C_s}$$

$$\frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = C_s$$

Capacitance
unit: Farad (F)

$$\frac{C_1 C_2}{C_2 + C_1} = C_s$$


$$R_s = R_1 + R_2 + \dots$$

Q is charge unit Coulomb


I is current unit Amp = $\frac{\text{Coulomb}}{\text{second}}$

$$\text{Power} = I \cdot V$$

(unit: Watt)

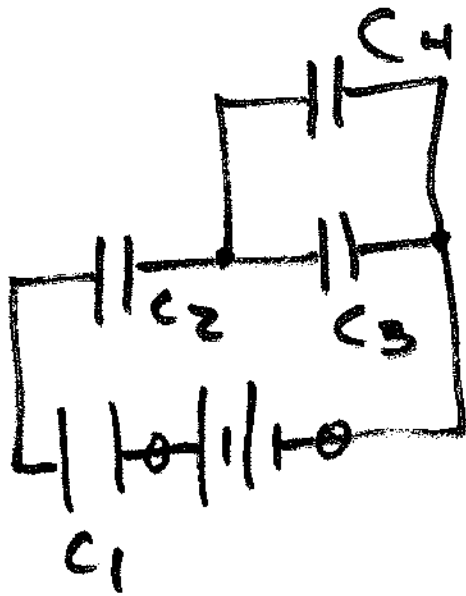


find equivalent C.

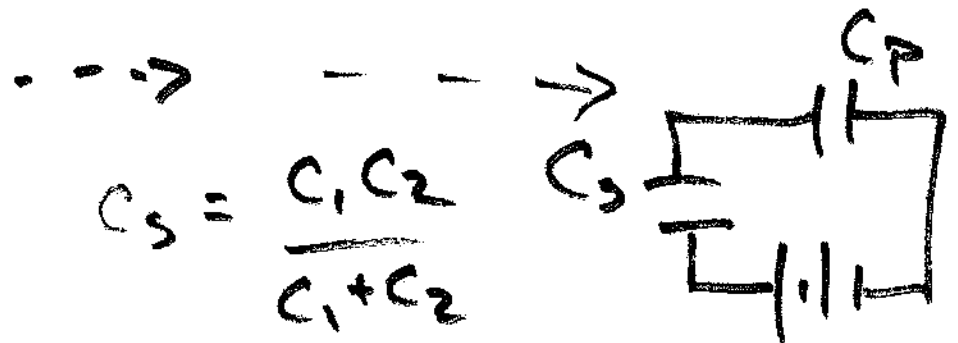

$$C_s = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{||} = C_p = C_3 + C_4$$
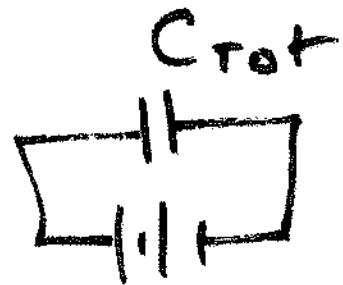
$$C_{\text{Tot}} = \frac{C_s C_p}{C_s + C_p}$$




Kirchoff's Laws of Circuits:

$$\sum_{\text{loop}} V = 0 \quad \text{loop rule}$$

$$\sum I_{\text{in}} = \sum I_{\text{out}} \quad \text{junction rule}$$

$$\underline{V = IR}$$

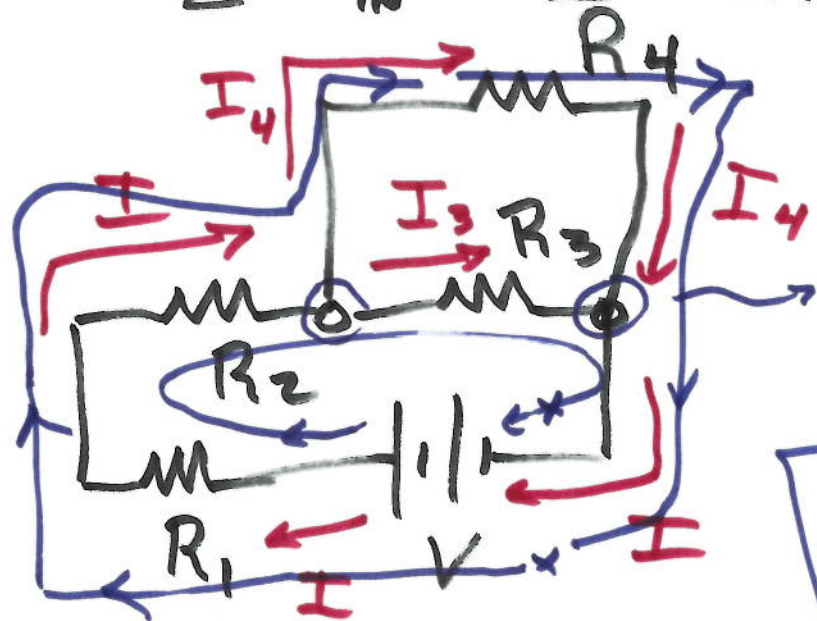

$$\begin{aligned} \sum I_{\text{in}} &= \sum I_{\text{out}} \\ I_3 + I_4 &= I \end{aligned}$$

$$\underline{\sum V_{\text{loop}} = 0} \quad \text{loop rule}$$

lower loop:

$$+V - IR_1 - IR_2 - IR_3 = 0$$

outer loop:

$$+V - IR_1 - IR_2 - I_4 R_4 = 0$$

Given: V, R_1, R_2, R_3, R_4

compute: I through each R .

$$\underline{I = I_3 + I_4}$$

$$V - I(R_1 + R_2) = I_3 R_3$$

$$\frac{V}{R_3} - I \frac{(R_1 + R_2)}{R_3} = I_3$$

Junc.

$$V - I(R_1 + R_2) = I_4 R_4 \quad \text{done.}$$

$$\frac{V}{R_4} - \frac{I(R_1 + R_2)}{R_4} = I_4$$

$$\frac{V}{R_3} - \overset{*}{I} \frac{(R_1 + R_2)}{R_3} + \frac{V}{R_4} - \overset{*}{I} \frac{(R_1 + R_2)}{R_4} = \overset{*}{I}$$

$$\frac{V}{R_3} + \frac{V}{R_4} = I \left(1 + \frac{R_1 + R_2}{R_3} + \frac{R_1 + R_2}{R_4} \right)$$

$$\frac{\frac{1}{R_3} + \frac{1}{R_4}}{1 + \frac{R_1 + R_2}{R_3} + \frac{R_1 + R_2}{R_4}} V = I \quad \text{mult. by } \frac{R_3 R_4}{R_3 R_4} \text{ to clean up:}$$

$$\frac{(R_4 + R_3) V}{R_3 R_4 + R_4 (R_1 + R_2) + R_3 (R_1 + R_2)} = I$$


Setting up the loops is most important!

When solving, draw (guess) each current, I , direction. Then draw each loop (with direction).

Power Supply:




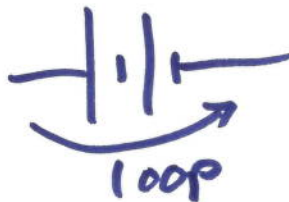$+V$ when loop "right way" through power supply (from $-$ to $+$).




$-V$ when backwards.

Resistor:

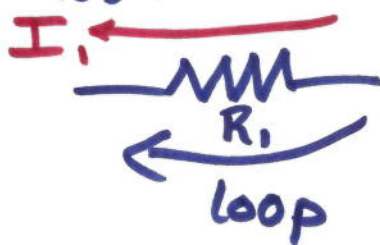


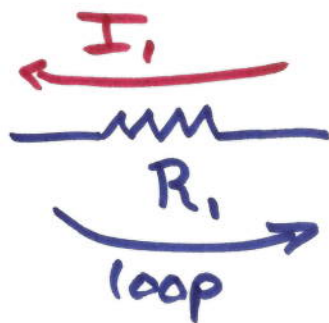$-IR$ when loop agrees with current direction.



$+IR$ when loop opposes direction of current.

BIG EXAMPLE of Kirchoff's Laws:

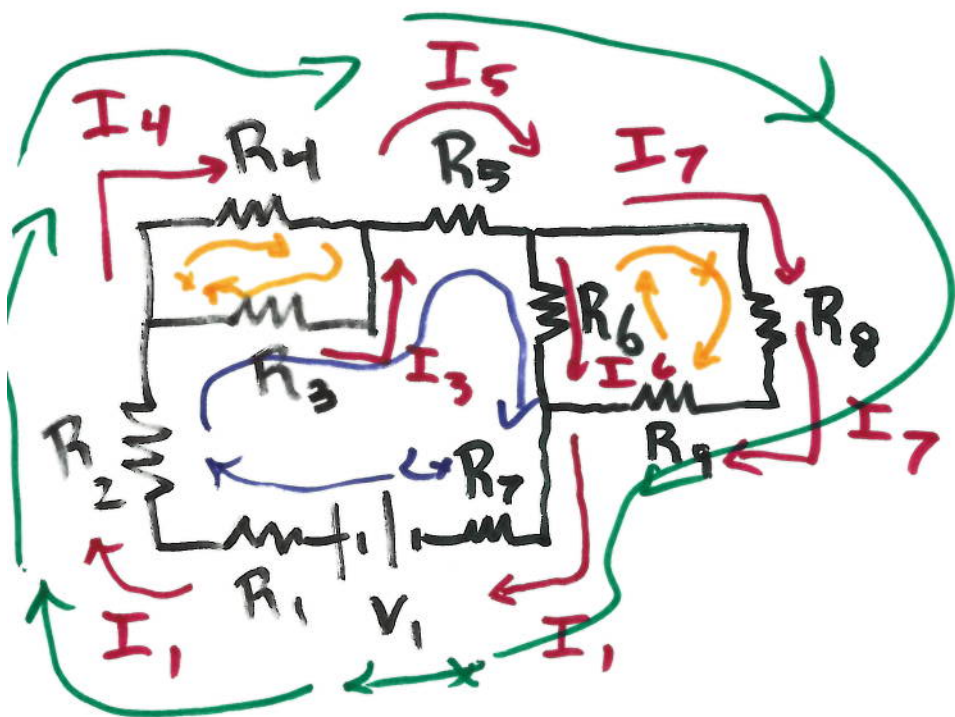

4 Junction Rules:

$$\left. \begin{array}{l} I_1 = I_3 + I_4 \\ I_3 + I_4 = I_5 \end{array} \right\} \text{Thus } I_1 = I_5$$

$$\left. \begin{array}{l} I_5 = I_6 + I_7 \\ I_6 + I_7 = I_1 \end{array} \right\} \text{Thus } I_1 = I_5$$

Enough Loops to hit every element once or more.

lower: $V_1 - I_1 R_1 - I_1 R_2 - I_3 R_3 - I_5 R_5 - I_6 R_6 - I_1 R_7$

outer:

$$V_1 - I_1 R_1 - I_1 R_2 - I_4 R_4 - I_5 R_5 - I_7 R_8 - I_7 R_9 - I_1 R_7 = 0$$

right loop:

$$-I_7 R_8 - I_7 R_9 + I_6 R_6 = 0$$

top loop:

$$-I_4 R_4 + I_3 R_3 = 0$$

This is enough to solve this system's I values given V and all R values.