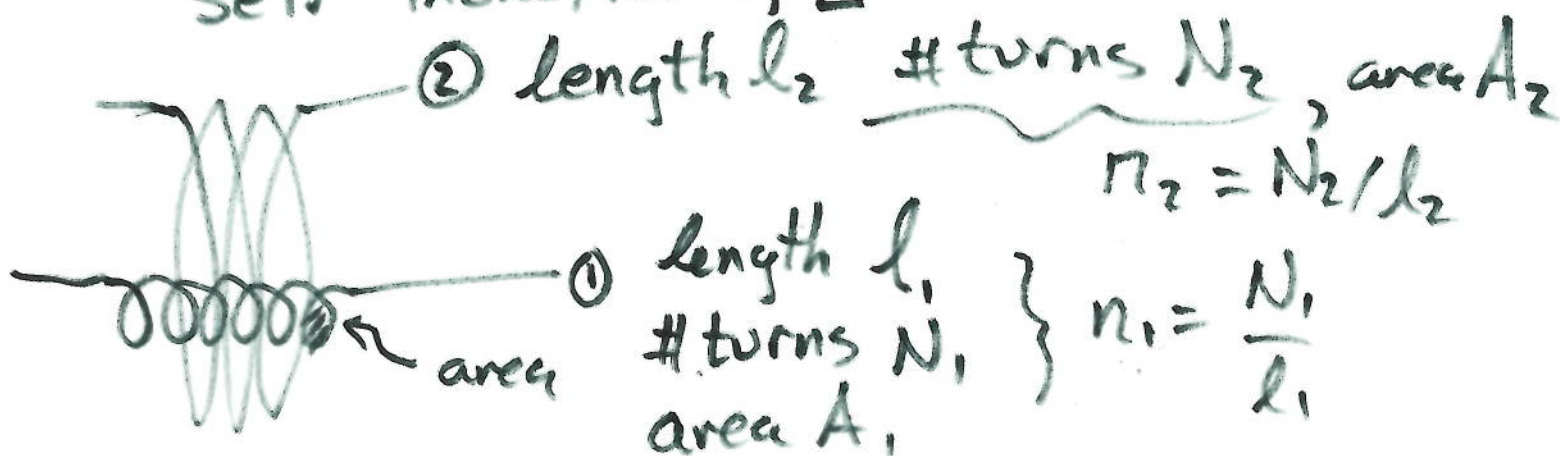


Inductance:

No Lab This Friday

Mutual Inductance, M

Self Inductance, L



There is V in ② due to changes in I_1 .

$$V_2 = - \frac{d\Phi_{B_2}}{dt} \quad \left. \begin{array}{l} \text{Faraday's} \\ \text{Law} \end{array} \right\} \quad \begin{array}{l} B = \mu_0 I n \\ \text{coil} \end{array} \quad n = \frac{N}{l}$$

We assume: B inside coils is $\mu_0 I n$ and 0 outside (approx).

$$\Phi_B = BAN$$

What is $\Phi_{B \text{ in } 2} = B_1 A_2 N_2$ due to 1?

$$V_2 = \frac{d}{dt} \Phi_{B_2} = A_1 N_2 \frac{\partial B_1}{\partial t}$$

$$B_1 = \mu_0 I_1(t) n_1$$

$$V_2 = \underbrace{A_1 N_2 \mu_0 n_1}_{M} \frac{\partial I_1(t)}{\partial t}$$

M
the Mutual Inductance

$$V_2 = M \frac{\partial I_1}{\partial t}$$

Can show $V_1 = M \frac{\partial I_2}{\partial t}$ with the same M.

$\Phi_{B_1} = B_2 A_1 (n_1 l_2)$
 due to 2 # of turns of 1 inside 2


$$B_2 = \mu_0 I_2 n_2$$

$$\Phi_{B_1} = \mu_0 I_2 n_2 \underbrace{A_1 n_1 l_2}_{N_2}$$

$$V_1 = M \frac{\partial I_2}{\partial t}$$

$$M = \mu_0 A_1 n_1 N_2 \quad \checkmark \text{ yay}$$

Self Inductance, L

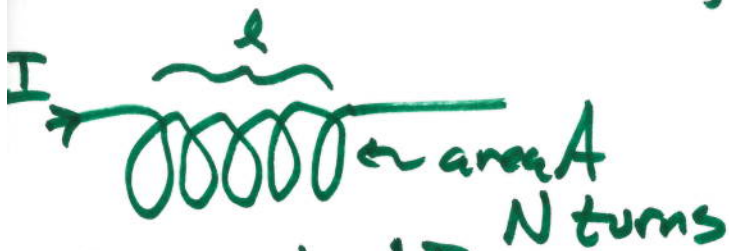

$$\Phi_B = BAN$$

$$B = \mu_0 I n$$

$$n = \frac{N}{l}$$

$$V = -L \frac{dI}{dt}$$

$$V = - \frac{d\Phi_B}{dt} = \underbrace{AN\mu_0 n}_{\substack{\text{Self-Inductance} \\ L}} \frac{dI}{dt}$$

$$L = \mu_0 AN^2 / l = \mu_0 A n N$$

100 turns coil 3cm length diameter 1.0cm.
Find L $\mu_0 = 4\pi \times 10^{-7} \frac{\text{Tm}}{\text{A}}$

$$A = \pi r^2$$

$$L = 3.3 \times 10^{-5} \text{ H}$$

$$\text{H} = \text{Henries} = \frac{1\text{V} \cdot \text{s}}{\text{A}} = 1\Omega \cdot \text{s}$$

Inductor as circuit element:

In DC: $V_L = -L \frac{dI}{dt}$


resists change in I , allows steady current through.

Compare with $V_C = \frac{Q(t)}{C}$ $Q = CV$
Capacitor:

resists DC (or steady) currents
allows rapidly changing AC

LR Circuit:

at $t=0$, close switch
find: $I(t)$

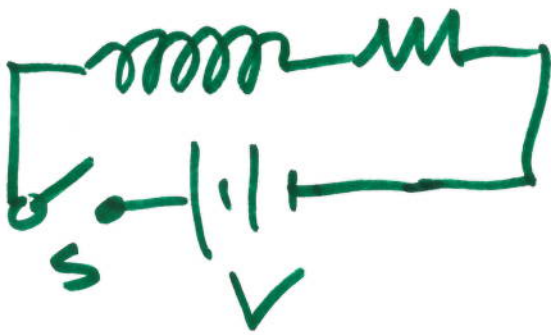

$$\sum_{\text{loop}} V = 0$$

$$V - L \frac{dI(t)}{dt} - IR = 0$$

Know: at $t=0$, $I=0$.

long time,  \rightarrow 

$$I_{\text{long time}} = \frac{V}{R}$$



try: $I(t) = I_{\infty}(1 - e^{-t/\tau})$

Show: $I_{\infty} = V/R$
and find τ .

$$\frac{dI(t)}{dt} = \frac{I_{\infty}}{\tau} e^{-t/\tau}$$

$$V - L \underbrace{\frac{I_{\infty}}{\tau} e^{-t/\tau}}_{dI/dt} - \underbrace{(I_{\infty}(1 - e^{-t/\tau}) R)}_{I(t)} = 0$$

$$V - I_{\infty}R - L \frac{I_{\infty}}{\tau} e^{-t/\tau} + I_{\infty}R e^{-t/\tau} = 0$$

$I_{\infty} = \frac{V}{R}$ yay!

for any t

$$\cancel{I_{\infty}R} = L \frac{\cancel{I_{\infty}}}{\tau}$$

$$\boxed{\tau = \frac{L}{R}}$$

Compare with $\tau = RC$ for RC Circuit.

Show: $\frac{\text{energy}}{\text{volume}}$ in \vec{B} is $\frac{B^2}{2\mu_0}$

$$\text{energy} = \int \text{Power} dt$$

$$\text{Power } P = IV$$

$$V \text{ inductor } L \frac{dI}{dt}$$

$$\text{energy} = \int I(t) L \frac{dI(t)}{dt} dt$$

clever ~~chain~~ rule application

$$E = \frac{1}{2} L I^2$$

integration by parts

$$\int u dv = uv - \int v du$$

$$u = I(t) \quad dv = \frac{dI}{dt} \quad \text{so } v = I$$

$$\int I dI = I^2 - \int I dI$$

$$2 \int I dI = I^2$$

$$\int I dI = \frac{1}{2} I^2$$

$$E = \frac{1}{2} L I^2 \quad \left(\text{compare } E = \frac{1}{2} C V^2 \right)$$

$$B = \mu_0 n I$$

plug in

Volume of coil

$$E = \frac{\cancel{l} A B^2}{2 \mu_0}$$

$$\boxed{\frac{E}{\text{Volume}} = \frac{B^2}{2 \mu_0}}$$